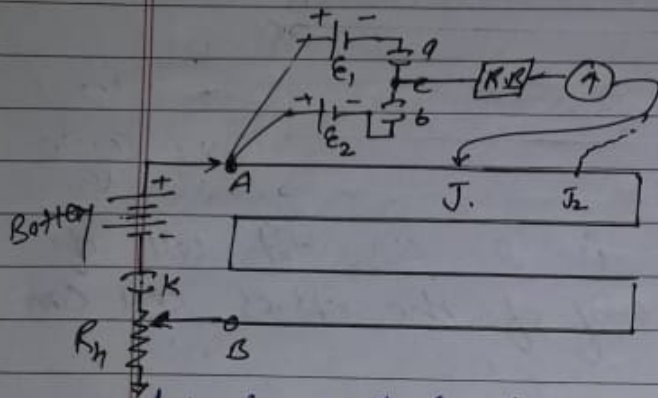


Application of potentiometer :-

Comparison of emfs of two primary cells :-

The circuit diagram for comparing the emfs is shown below fig.



Let E_1 and E_2 be the emfs of two primary cells which are to be compared. The positive terminals of these cells are connected to the end A of the potentiometer wire and their negative terminals are connected to a high resistance box R.B., a galvanometer G and jockey J through a two way key.

If the plug is inserted b/w 'a' and 'c' the cell E_1 gets introduced in the circuit. The jockey J is moved along wire AB till the galvanometer shows no deflection.

Let the position of the jockey is J_1 and length of wire l_1 . Then according to principle of potentiometer

$$E_1 = K \cdot l_1 \quad \text{--- (1)}$$

If the plug is inserted b/w 'b' and 'c' the null point again obtained for cell E_2 .

let the balancing length l_2 , then

$$E_2 = K l_2 \quad \text{--- (2)}$$


Hence,
$$\frac{E_1}{E_2} = \frac{K l_1}{K l_2}$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

if one of the two cell is a standard cell of known emf, the emf of the other cell can be determined.

$$E_2 = E_1 \cdot \frac{l_2}{l_1}$$

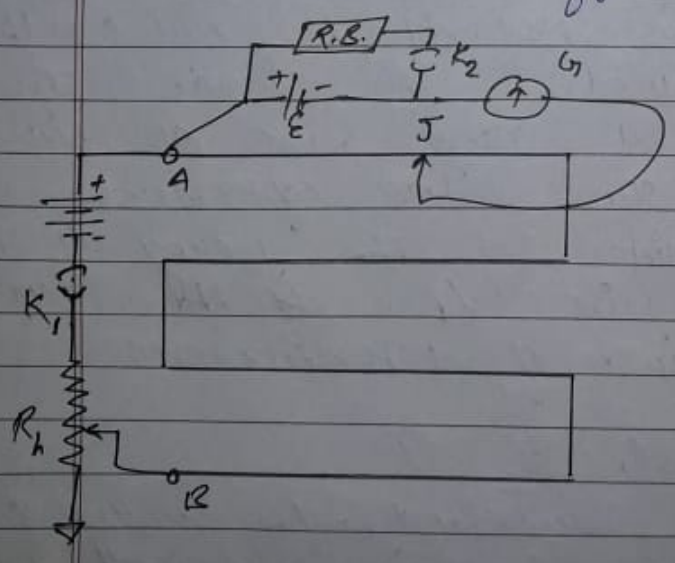2. Internal resistance of a primary cell by a potentiometer. The circuit diagram shown in below fig.



The positive terminal of the cell of emf \mathcal{E} whose internal resistance r is to be measured is connected to the end A of the potentiometer wire and its negative terminal to a galvanometer G and a jockey J. A R.B. resistance box connected across the cell through the key K_2 .

If close the key K_1 and K_2 kept open. move the Jockey along wire AB till it balances the emf \mathcal{E} of the cell. let l_1 is the balancing length of wire then

$$\mathcal{E} = k l_1 \quad \text{--- (1)}$$

If close the key K_2 find the if l_2 is the balancing length then

$$V = k l_2 \quad \text{--- (2)}$$

Thus

$$\frac{\mathcal{E}}{V} = \frac{l_1}{l_2}$$

If current I flows through the cell when it is shunted with resistance R then by ohm's law

$$\mathcal{E} = I(R+r) \quad \& \quad V = IR$$

$$\frac{\mathcal{E}}{IR} = \frac{l_1}{l_2}$$

$$1 + \frac{r}{R} = \frac{l_1}{l_2}$$

$$\frac{r}{R} = \frac{l_1}{l_2} - 1$$

hence

$$r = R \left[\frac{l_1}{l_2} - 1 \right]$$

Sensitivity of a potentiometer :-

A potentiometer is sensitive if
(i) it is capable of measuring very small potential differences.

(ii) it shows a significant change in balancing length for a small change in the potential difference being measured.

Note :- Smaller the potential gradient, Greater will be the sensitivity of the potentiometer.